


EXP NO 5:- Simulation of CMOS Inverter Switching Characteristics in winspice

Name: Balabhadruni Sumanth	Date: 16/07/21
Roll No: CB-EN04ECE18211	Marks: out of 15


Aim:-

Obtain the voltage transfer characteristics for a CMOS inverter and also plot the output current using winspice.

Circuit Diagram:-

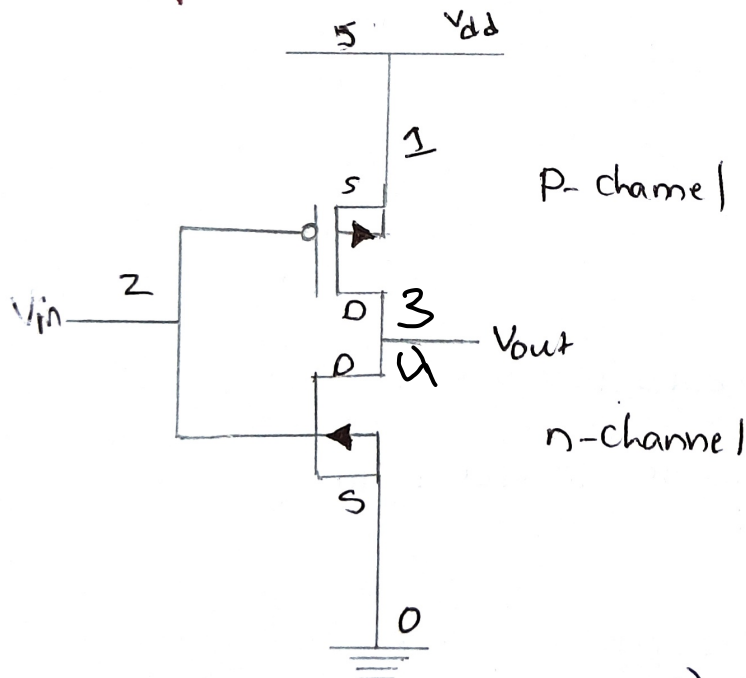

CMOS Inverter:-

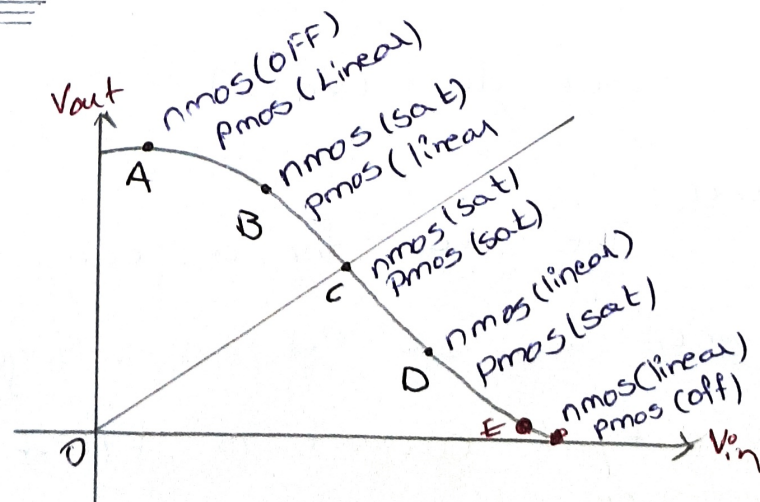

CODE:-

VTC:-

* VTC graph For CMOS Inverter

Vg 2 0 DC 2V

Vdd 1 0 DC 5V

mp 3 2 11 modp w=5u L=1u

mn 3 2 0 0 modn w=2u L=1u

.dc Vg 0 5 0.01

.plot dc v(3) {v(2)}

output Current

* Inverter char

Vdd 1 0 dc 5

Vin 2 0 dc 0

mp 3 2 1 1 modp w=10u l=1u


mn 4 2 0 0 modn w=4u l=1u

Vdum 3 4 0


.dc Vin 0 5 0.01

.plot dc i (Vdum)

VTC GRAPH:

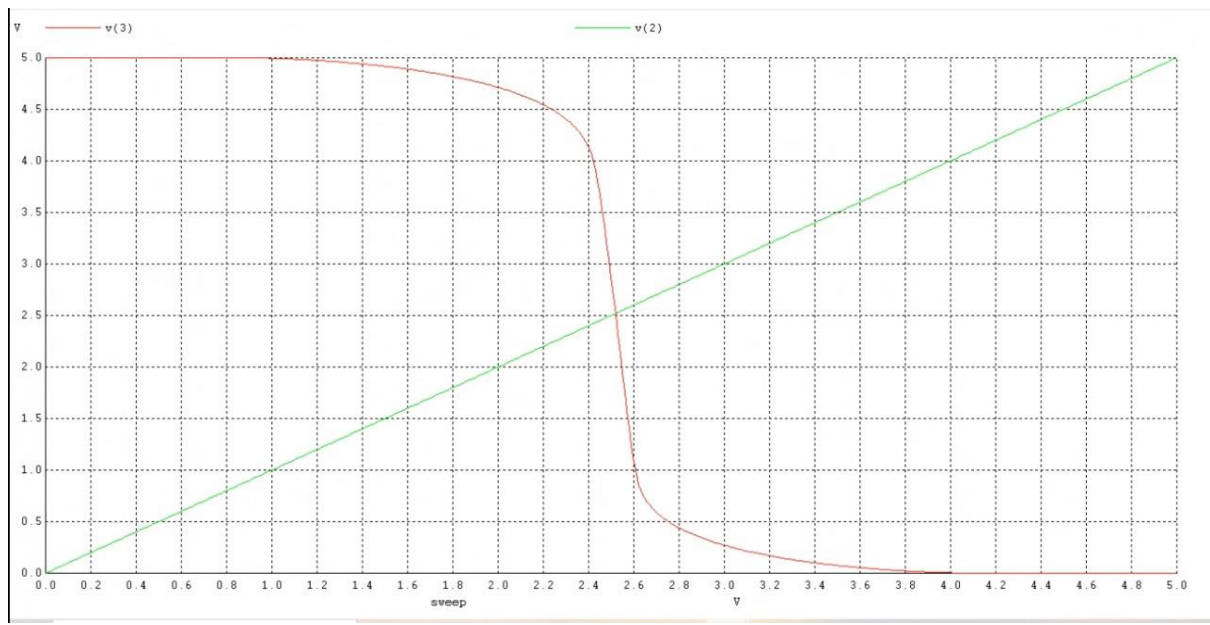

CURRENT GRAPH:

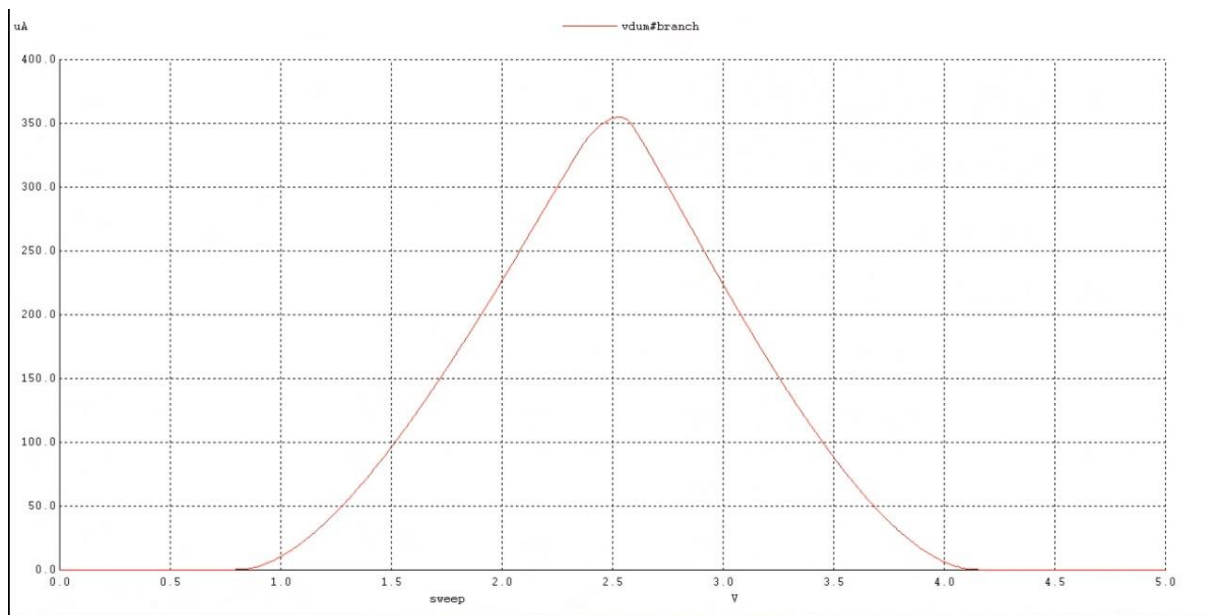

Inference:-

The VTC for a CMOS inverter was obtained and the Mid point voltage is $2.5V$ and the output current is plotted and verified using win spice